

Contents

1	Continuous-Time Systems	1
1.1	Relations in the Time Domain	1
1.2	Relations in the Frequency Domain	2
1.2.1	The Laplace Transform	3
1.2.2	The Fourier Transform	5
1.3	Transfer Functions	7
2	Analog Filters	13
2.1	The Ideal Low-Pass Filter	13
2.2	Butterworth Filters	15
2.3	Chebyshev Filters	19
2.4	Inverse Chebyshev Filters	24
2.5	Elliptic Filters	27
2.6	Bessel Filters	33
2.7	Filter Transformations	41
2.7.1	Low-Pass High-Pass Transformation	42
2.7.2	Low-Pass Bandpass Transformation	43
2.7.3	Low-pass Bandstop Transformation	45
2.7.4	Filter Transformations in Practice	46
3	Discrete-Time Systems	51
3.1	Discrete-Time Convolution	52
3.2	Relations in the Frequency Domain	54
3.3	The z -Transform	58
3.3.1	Definition of the z -Transform	58
3.3.2	Properties of the z -Transform	59
3.3.3	Examples	61
3.4	Stability Criterion in the Time Domain	65
3.5	Further Properties of the Unit-Sample Response $h(n)$	66
4	Sampling Theorem	69
4.1	Introduction	69
4.2	Sampling	69
4.3	Band-Limited Signals	71
4.4	Practical Aspects of Signal Conversion	74
4.4.1	Analog-to-Digital Conversion	74

4.4.2	Digital-to-Analog Conversion	76
4.5	Mathematical Analysis of the D/A Conversion Process.....	77
5	Filter Structures.....	83
5.1	Graphical Representation of Discrete-Time Networks.....	83
5.2	FIR Filters	86
5.2.1	The Basic Structure of FIR Filters	86
5.2.2	Poles and Zeros of the FIR Filter	89
5.2.3	Linear-Phase Filters	91
5.3	IIR Filters	95
5.3.1	An Introductory Example.....	95
5.3.2	Direct-Form Filters	96
5.3.3	Poles and Zeros.....	98
5.4	Further Properties of Transfer Functions.....	101
5.4.1	Stability Considerations in the Frequency Domain.....	101
5.4.2	Minimum-Phase Filters	103
5.5	State-Space Structures.....	104
5.6	The Normal Form	109
5.7	Digital Ladder Filters.....	110
5.7.1	Lossless Networks	112
5.7.2	Realisability.....	113
5.7.3	Kirchhoff Ladder Filters.....	114
5.7.4	Wave Digital Filters.....	120
5.7.4.1	Wave Parameters	120
5.7.4.2	Decomposition of the Analog Reference Network into One-Ports and Multi-Ports.....	126
5.7.4.3	The Reflectance of Capacitor and Inductor	130
5.7.4.4	The Role of the Bilinear Transform	133
5.7.4.5	Observance of the Realisability Condition	135
5.7.4.6	Second-Order Wave Digital Filter Block	138
6	Design of IIR Filters.....	141
6.1	Introduction	141
6.2	Preservation Theorem of the Convolution.....	142
6.3	Approximation in the Time Domain	144
6.3.1	Impulse-Invariant Design	145
6.3.2	Step-Invariant Design	151
6.3.3	Ramp-Invariant Design	154
6.4	Approximation in the Frequency Domain	156
6.4.1	Difference Method	157
6.4.2	Bilinear Transform.....	160
6.4.3	Practical Filter Design Using the Bilinear Transform	165
6.4.4	IIR Filter with Bessel Characteristics.....	169
6.4.4.1	Design with Prescribed Delay t_0	172
6.4.4.2	Design with Given 3-dB Cutoff Frequency.....	173

7	Design of FIR Filters	177
7.1	Introduction	177
7.2	Linear-Phase Filters	178
7.3	Frequency Sampling	181
7.4	Minimisation of the Mean-Square Error	188
7.4.1	Direct Solution	191
7.4.2	The Window Method	198
7.5	Chebyshev Approximation	203
7.5.1	The Remez Exchange Algorithm	203
7.5.2	Polynomial Interpolation	206
7.5.3	Introduction of a Weighting Function	210
7.5.4	Case 2, 3 and 4 Filters	213
7.5.5	Minimum-Phase FIR Filters	215
7.6	Maximally Flat (MAXFLAT) Design	219
8	Effects of Finite Register Length	227
8.1	Classification of the Effects	227
8.2	Number Representation	227
8.2.1	Fixed-Point Numbers	228
8.2.2	Floating-Point Numbers	231
8.3	Quantisation	233
8.3.1	Fixed-Point Numbers	233
8.3.2	Floating-Point Numbers	238
8.4	System Noise Behaviour	241
8.4.1	Signal-to-Noise Ratio	241
8.4.2	Noise Filtering by LSI Systems	243
8.4.3	Optimum Use of the Dynamic Range	245
8.5	Noise Optimisation with Fixed-Point Arithmetic	247
8.5.1	Noise Behaviour of First- and Second-Order Filter Blocks	247
8.5.2	Shaping of the Noise Spectrum	255
8.5.3	Noise in a Cascade of Second-Order Filter Blocks	260
8.6	Finite Coefficient Wordlength	264
8.6.1	Coefficient Sensitivity	265
8.6.2	Graphical Representation of the Pole Density	267
8.6.3	Increased Pole Density at Low and High Frequencies	272
8.6.4	Further Remarks Concerning Coefficient Sensitivity	277
8.6.5	A Concluding Example	278
8.7	Limit Cycles	281
8.7.1	Nonlinearities in Actual Implementations	282
8.7.2	Stability of the Linear Filter	284
8.7.3	Stability with Quantisation and Overflow Correction	289
8.7.4	A Constructive Approach for the Determination of Stability	290
8.7.4.1	The Linear System	290
8.7.4.2	Stability of the Nonlinear System	292
8.7.5	A Search Algorithm in the State Plane	304
8.7.6	Summary	311

9	Oversampling and Noise Shaping.....	313
9.1	D/A Conversion.....	313
9.1.1	Interpolation	314
9.1.2	Noise Filtering.....	316
9.1.3	Noise Shaping.....	317
9.2	A/D Conversion.....	320
9.2.1	Oversampling and Decimation	320
9.2.2	Noise Filtering.....	322
9.2.3	Oversampling $\Delta\Sigma$ Converter.....	323
10	Appendix	327
10.1	Symbols and Abbreviations.....	327
10.2	References	329
10.3	Filter Design Tables	331
10.4	Filter Design Routines.....	346
	Index.....	359